
 
 


Summary of Lecture I

 


```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
```

```
entity AND_Gate is
  Port ( A : in STD_LOGIC;
        B : in STD_LOGIC;
        C : out STD_LOGIC);
end AND_Gate;
```


```
architecture Behavioral of AND_Gate is
```

```
begin
  C <= A and B;
```


```
end Behavioral;
```

 


VHDL

 

Character	Value
'U'	uninitialized
'X'	strong drive, unknown logic value
'0'	strong drive, logic zero
'1'	strong drive, logic one
'Z'	high impedance
'W'	weak drive, unknown logic value
'L'	weak drive, logic zero
'H'	weak drive, logic one
'_'	don't care

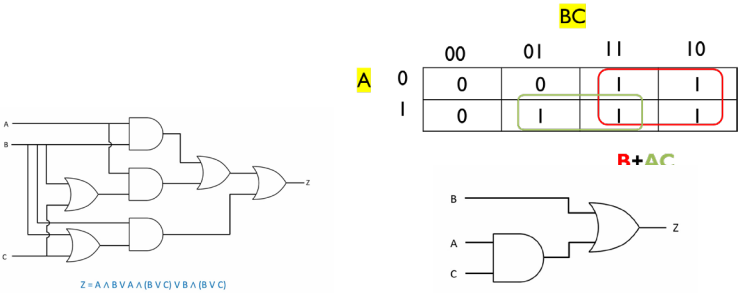

Summary of lecture 2

 

Processor with Multiple Instruction Execution Units


 
 
 
 


Figure 3-4: FPGA with Multiple Instruction Execution Units







■ Concurrent and Sequential statements

 - Conditional signal assignment (when)
- Selected Signal Assignment (with select)
- Process statement (if/else)
- Process statement (case)





Summary of lecture 3

Signal and Variables

   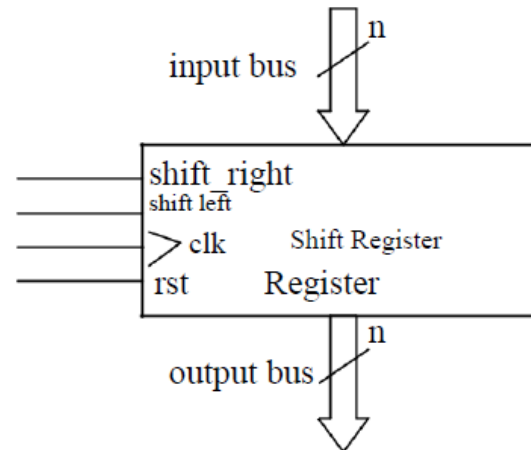  


Summary of lecture 4


Operators	VHDL
Equality & Relational	=
	/=
	<
	<=
	>
Logical	>=
	not
	and
	or

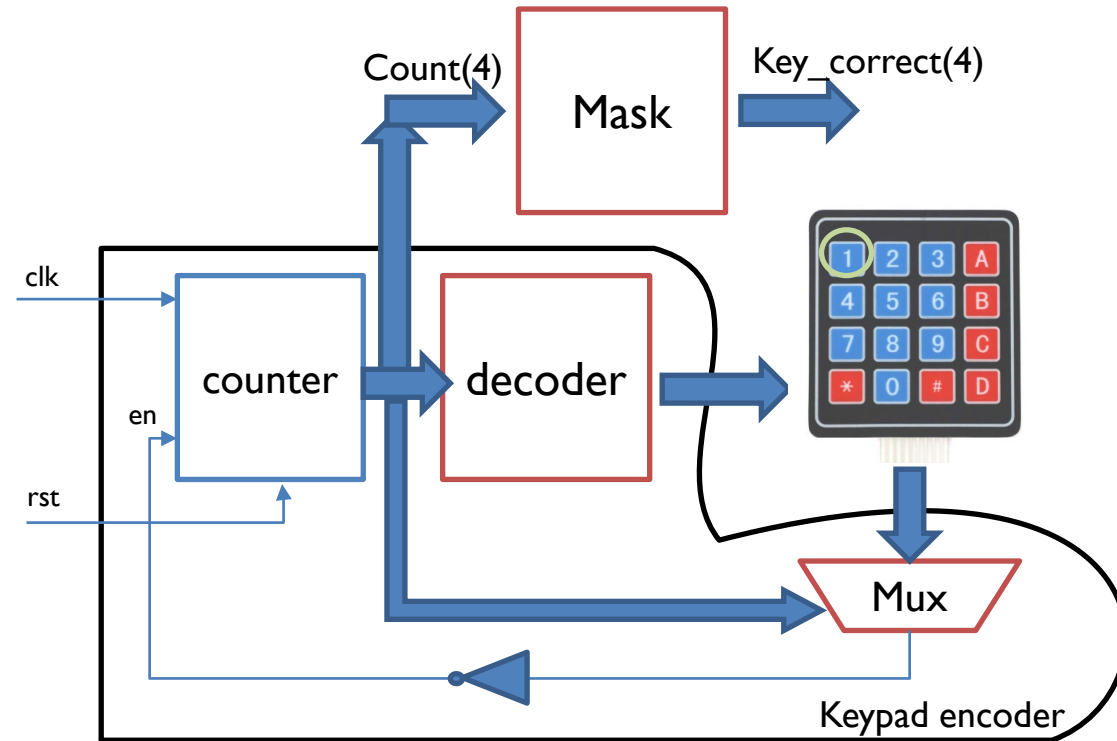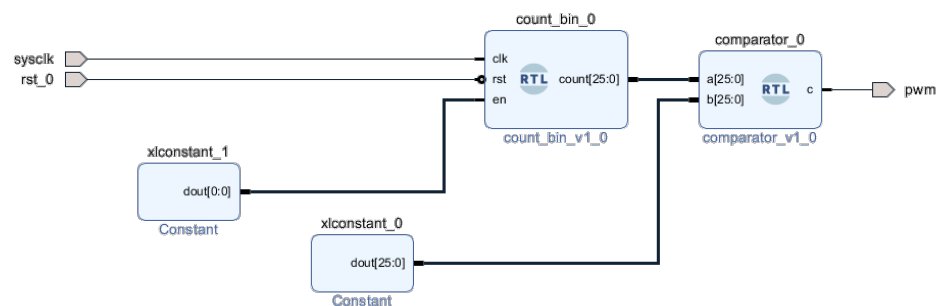


Summary of lecture 5

 


- **Ripple-carry adder**

 

- **Carry-look-ahead adder**

 


- **Full Adder/Subtractors**

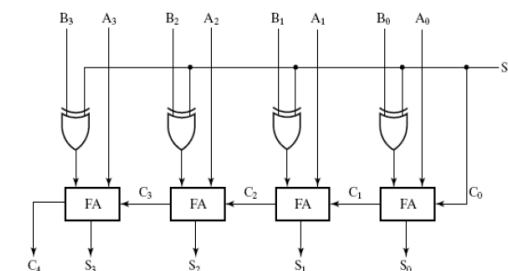


Summary of lecture 5

- Multiplier

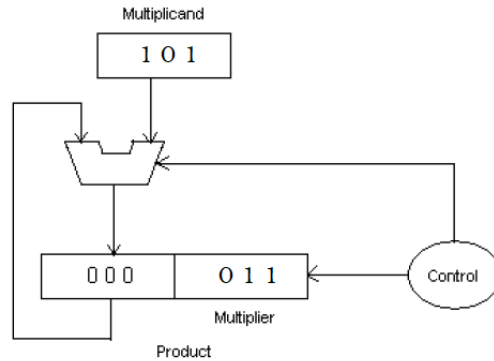


- Array Multiplier

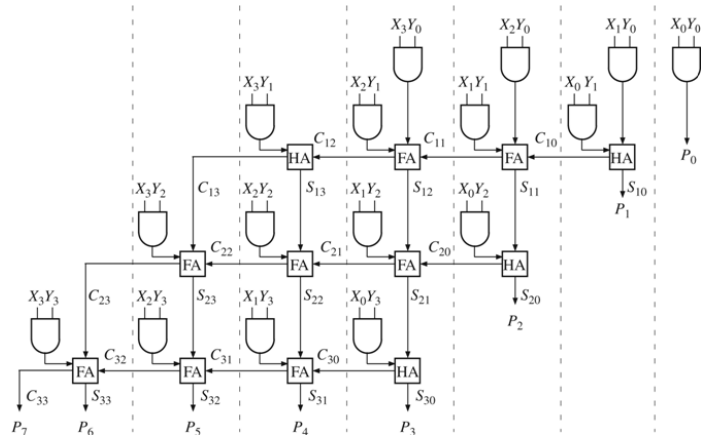


- Dividers

- Clk divider
- Division by subtraction
- Division by multiplication

- Fixed point

 


- Floating point





 


Summary of lecture 6


■ Moore

 









■ Mealy

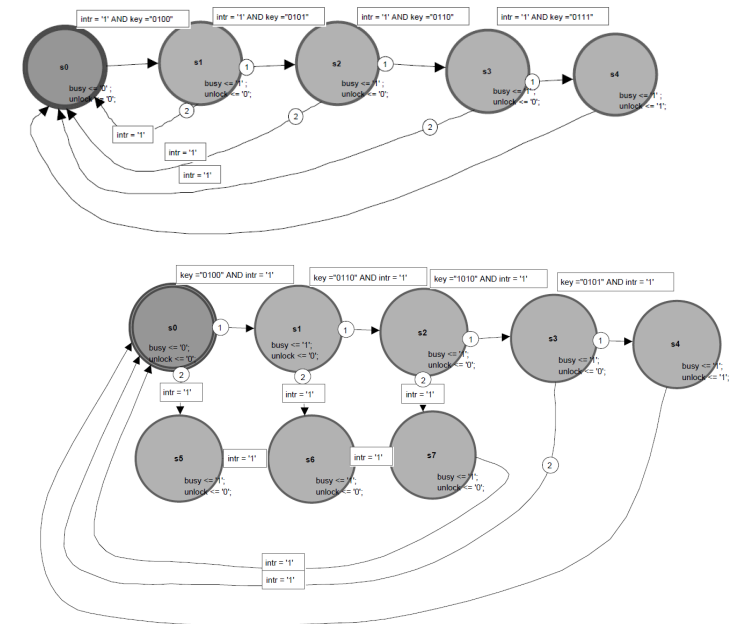    

Summary of lecture 6


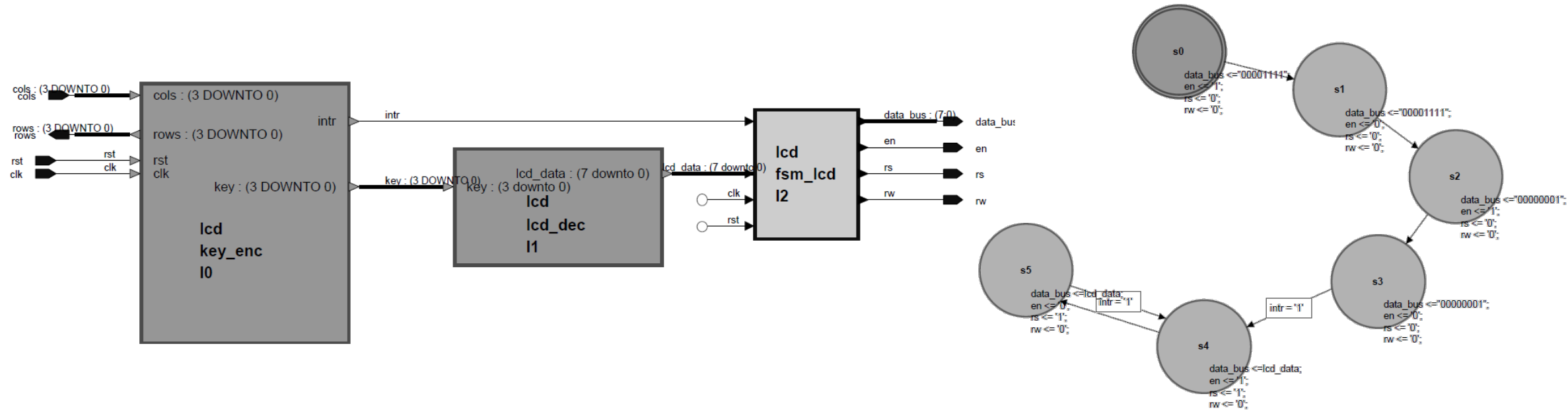


Summary of lecture 7

        

Summary of Lecture 8



■ CPLD

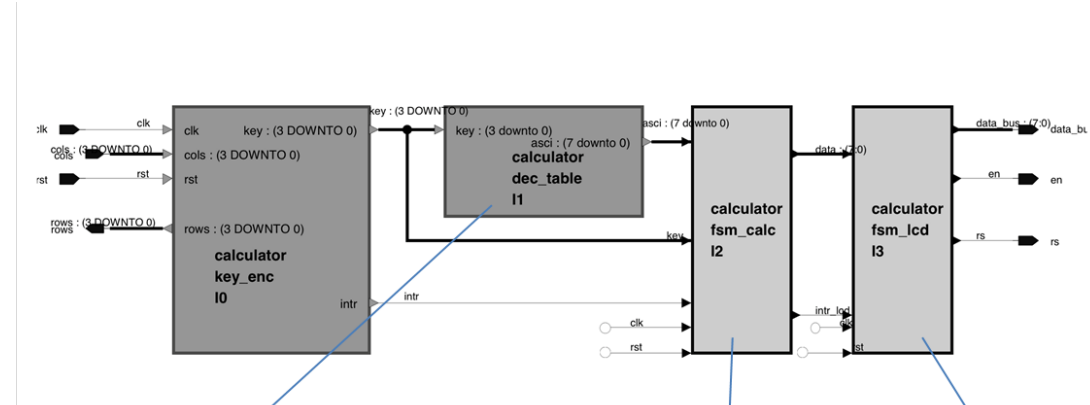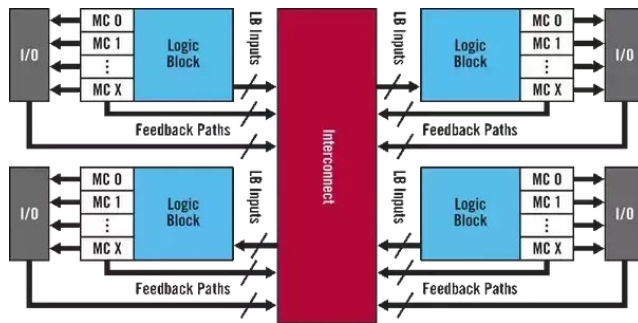



```

ENTITY dec_table IS
-- Declarations
  port(key: in std_logic_vector(3 downto 0);
        ascii: out std_logic_vector(7 downto 0));
END dec_table ;

-- hds interface end
ARCHITECTURE rtl OF dec_table IS
BEGIN
  process(key)
  begin
    if(key="0000")then ascii<="00110000";
    elsif(key="0001")then ascii<="00110001";--0
    elsif(key="0010")then ascii<="00110010";
    elsif(key="0011")then ascii<="00110011";
    elsif(key="0100")then ascii<="00110100";
    elsif(key="0101")then ascii<="00110101";
    elsif(key="0110")then ascii<="00110110";
    elsif(key="0111")then ascii<="00110111";
    elsif(key="1000")then ascii<="00111000";
    elsif(key="1001")then ascii<="00111001";--9
    elsif(key="1010")then ascii<="00110101";--+
    elsif(key="1011")then ascii<="00110110";-- -
    elsif(key="1100")then ascii<="00101010";-- *
    elsif(key="1101")then ascii<="00101111";--^2
    elsif(key="1110")then ascii<="00101110";--.
    else ascii<="00111101"; --=
    end if;
  end process;
END rtl;
  
```

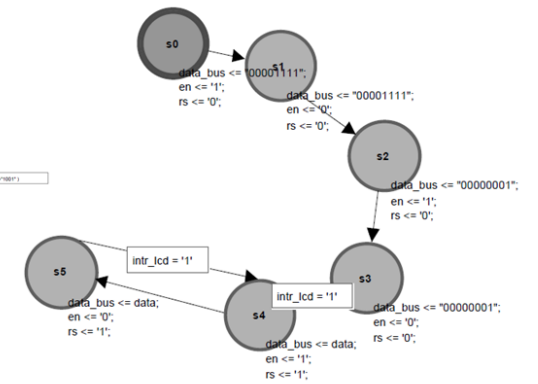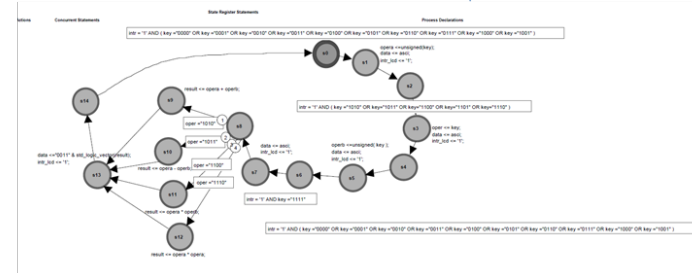


Summary of lecture 9

  


Summary of lecture 10



UART

 

SPI

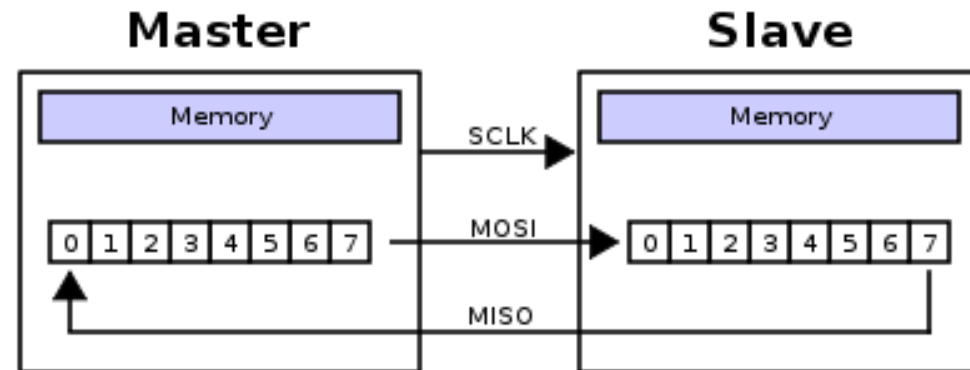


I2C

  


Summary of lecture 11

Error detection:



- Parity check

 

Checksum

 

CRC

  

Summary of lecture 11

- Quality Metrics of a Digital Design
- Performance
- Propagation delay
- Metastable
- Clock Skew

